



Universal Rotator

Instructions:

1. Use structural modelling for this experiment; means instantiate components and use port map to connect those components.
2. In pen paper design use proper labeling for each wire. And use same labels for the VHDL code.
3. Perform RTL simulation using the given testbench and tracefile.
4. Evaluate your design on Max-10 board.

Problem Statement:

1. Design

Design a universal rotator circuit, which can perform logical right rotate or left rotate on 8-bit input by the specified number of bits.

 


Figure 1: Block diagram

For $L = 0$, output will be right rotated version of input.
For $L = 1$, output will be left rotated version of input.

Figure(2) is the design of right shift by 4 block. Similarly you should design right rotate by 4 block, right rotate by 2 block and right rotate by 1 block.

 


Figure 2: Right shift by 4 bits

The output of shift block in figure(2) will be a7 a6 a5 a4 a3 a2 a1 a0 for b2 = 0.
For b2 = 1 its output will be 0 0 0 0 a7 a6 a5 a4.

2. VHDL description

Describe your designed circuit in VHDL. Block in figure(2) can be described in VHDL as follows

```
n4_bit : for i in 0 to 7 generate
lsb: if i < 4 generate
b2: mux port map(I(0) => a(i), I(1) => a(i+4), S => b(2), Y => s(i));
end generate lsb;
msb: if i > 3 generate
b2: mux port map(I(0) => a(i), I(1) => '0', S => b(2), Y => s(i));
end generate msb;
end generate ;
```

You need to design the mux used in the above code using logic gates from Gates.vhdl.
Similarly you can describe Right rotate by 4 bits, 2 bits, 1 bit and Bit reversal block.

3. Simulation

Simulate your design using the generic testbench to confirm the correctness of your description.
To do this, use the tracefile given below and modify the testbench given to you appropriately.

Tracefile format: (< L B2 B1 B0 A7 A6 A5 A4 A3 A2 A1 A0 > < S7 S6 S5 S4 S3 S2 S1 S0 > 11111111)
[Tracefile](#)

4. Testing of Board using scanchain

Perform scanchain based testing using Max-10 board.